

Roll No. ....

Total Pages : 4

**2204/M**

**K-33/2051**

**BASIC ELECTRICAL ENGINEERING**

Paper–DECE-101

Semester–II

Time allowed : 3 Hours] [Maximum Marks : 50

**Note:** The candidates are required to attempt three questions each from section A and section B carrying 5 marks each and the entire section C consisting of 10 questions carrying 2 marks each.

**SECTION-A**

1. Write a short note on : 5
  - (i) Magnetic leakage
  - (ii) Fringing.

2. Four resistances 56 , 50 , 40 and R are in parallel across a d.c. supply. Current in 56 resistance is 5A and the total supply current is 37.6 A. Find R. 5
3. Discuss the concept of constant current source with graphical representation of the characteristics of ideal and practical current sources. 5
4. State and explain Fleming's Left hand Rule. 5

**SECTION-B**

5. Define cycle, frequency, waveform, r.m.s. value and average value of an alternating quantity. 5
6. Why power factor is required to be improved, mention the advantages of improved power factor? 5
7. A 50 Hz voltage of 115 (r.m.s. value) is applied across a 70 resistance :

- (i) Write the equations for the voltage and the resulting current. 3
- (ii) Draw voltage and current waveforms. 2
8. Explain the concept of resonance in R-L-C Series Circuit. 5

### SECTION-C

9. All questions are compulsory : 10×2 = 20
- (i) Define Branch in an electrical circuit.
- (ii) What is meant by the term single phase circuit?
- (iii) Two identical coils with  $L = 0.03$  H have a coupling coefficient of 0.8. Calculate the mutual inductance.
- (iv) State Kirchoff's Current Law.
- (v) Define magnetic flux (  $\Phi$  ) and magnetic flux density (B).

- (vi) Draw power triangle. Also mention the units.
- (vii) On what factors resistance depends? Explain.
- (viii) Write any two points of comparison between magnetic and electric circuit.
- (ix) Define Capacitive Reactance. Give its units.
- (x) Can we use Ohm's law for AC circuits?